

Lab 0

Lab orientation

Shahed Ahmed

Date: 1/20/2023

CDA 3203 Computer Logic Design

Spring 2023

Dr. Maria Petrie

Florida Atlantic University

Circuit Simulation Results

Using Altera Quartus II Web Edition 9.1 to simulate a circuit for the equation $Y=A*B'+C'$

Schematic

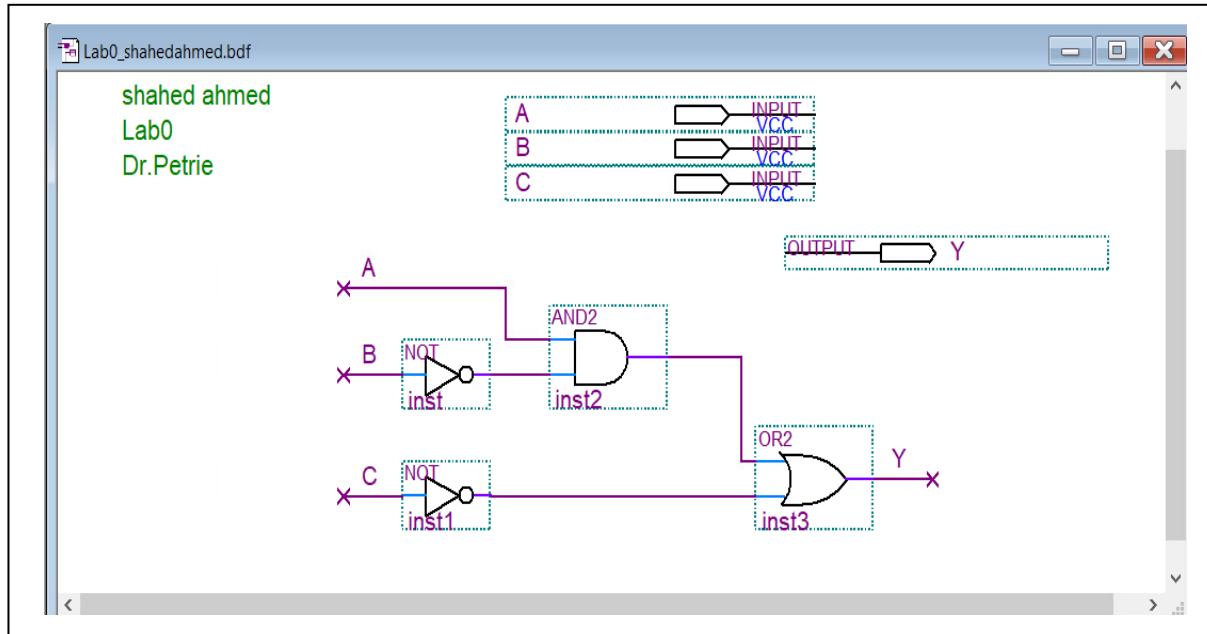


Figure 1: Enter your description HERE

Timing Diagram

